

DEVICES AND COMMUNICATION BUSES FOR DEVICES NETWORK–

Lesson-8: Parallel Port Interfacing with Stepper Motor

Port Interfacing — Parallel port outputs O0 to O7

- Four outputs may be used as driver to four coils of a stepper motor

Stepper-motor rotation

- One step angle when its four coils are given the currents in a specific sequence and that sequence is altered.
- Assume that currents at an instance equal $+i, 0, 0, 0$ in four coils X, X', Y, Y' . The motor rotates by one step when the currents change to $0, +i, 0, 0$.

Forward motion Sequences at the intervals of T

- Sequences at the intervals of T are changed as follows: 1000, 0100, 0010, 0001, 1000, 0100, [The bits in the nibble (set of 4 bits) rotate by right shift.]
- Here 1 corresponds to $+i$. The motor rotates n step angles in interval $= (n.T)$.

Reverse motion Sequences at the intervals of T

- Sequences are changed to rotate the motor in reverse direction
- 0001, 00010, 0100, 1000, 0001, 0010,[The bits in the nibble (set of 4 bits) rotate by left shift.]

Half Angle Change

- Coils are given the currents in the sequences of 1100, 0110, 0011, 1001, 1100, 0110, or 0011, 0110, 1100, 1001, 0011, 0110,
- The motor rotates $(n/2)$ steps in interval $= (n.T/2)$. T is the period of clock pulses, which drive the motor by change of coil currents to next sequence.


Port Interfacing

- 4 coils connect to parallel-port 4 outputs

Stepper motor driver— a processing element

- **Driver** is given two outputs from the port— clock pulses and rotating direction bit r . For example, if $r = 1$, the motor rotates clockwise and 0 then anti-clockwise. The motor rotates as long as clock pulses are given at the output pin.

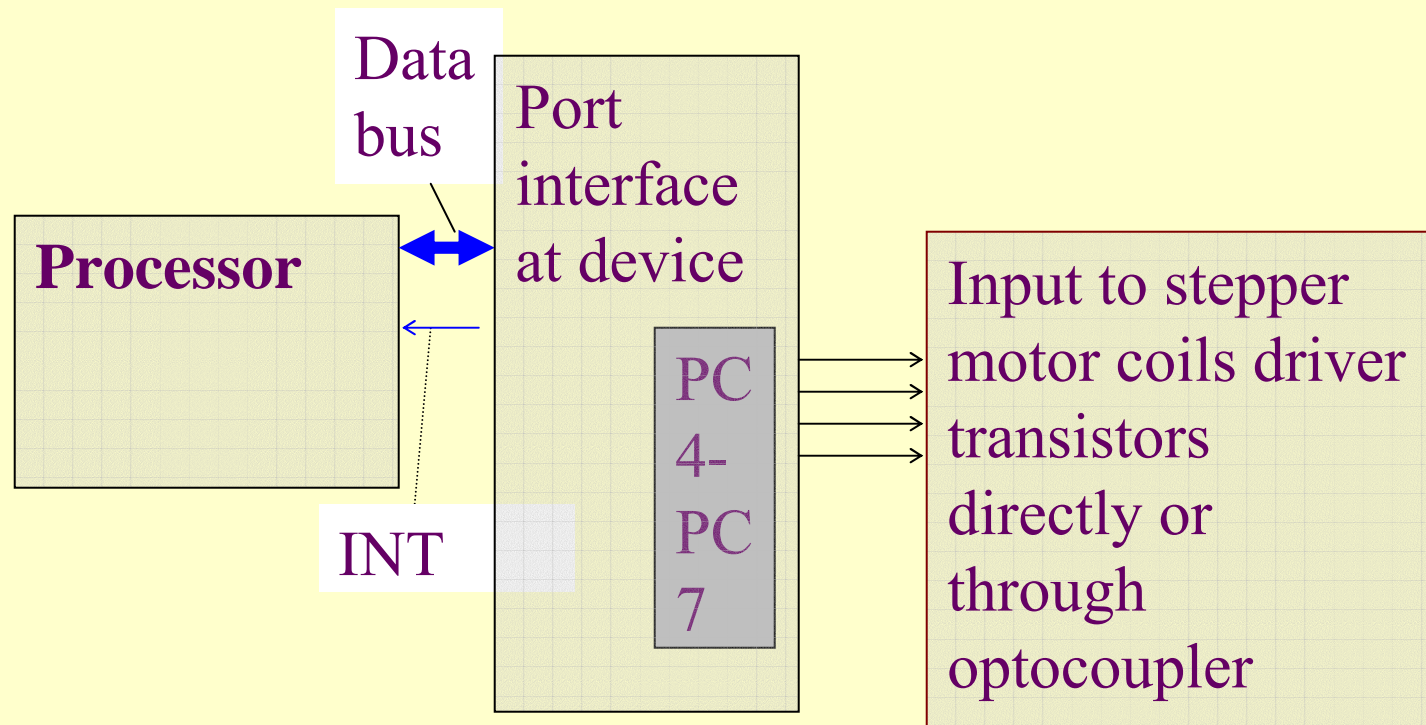Four-bit parallel output port C connected to a stepper motor



Summary

We learnt

- Stepper motor four coils
- Sequences of current inputs to the coils
- 1000, 0100, 0010, 0001, 1000, 0100,
Full step forward
- 0001, 00010, 0100, 1000, 0001, 0010,
Full step reverse
- 1100, 0110, 0011, 1001, 1100, 0110,
Half step forward
- 0011, 0110, 1100, 1001, 0011, 0110,
Half step reverse

End of Lesson 8 of Chapter 3